

Total number of printed pages-3

3 (Sem-1) CSC M2

2021

(Held in 2022)

COMPUTER SCIENCE

(Major)

Paper : 1·2

(Basic Electronics)

Full Marks : 60

Time : Three hours

***The figures in the margin indicate
full marks for the questions.***

Answer any six questions.

1. Give reasons for the following : 5+5=10

(a) The temperature coefficient of resistance of a semiconductor is negative while that of a metal is positive.

(b) A semiconductor behaves as an insulator at 0K while it has some conductivity at room temperature.

Contd.

2. (a) In a silicon $p-n$ junction, calculate the increase in voltage across the diode if the forward current is doubled. Assume $V_T = 26\text{ mV}$.

(b) If the current flowing through a $p-n$ junction diode increases ten times, what is the increase in diode voltage? Assume forward biased silicon diode operating at room temperature.

5+5=10

3. Considering three logic variables A , B and C , write the fundamental properties of Boolean algebra. 10

4. (a) State and prove De Morgan's theorem.

(b) Prove the following Boolean identities :

(i) $AB + A\bar{B} = A$

(ii) $A(A + B) = A$

10

5. Find the POS and SOP forms of the following expression :

$$X = \sum m(0, 1, 3, 6, 7, 8, 13, 15)$$

Which one is more cost-effective? 10

6. What is the shortcoming of an S-R flip-flop? Explain how this shortcoming is removed in J-K flip-flop. 10

7. Write short notes on : (*any two*)

5×2=10

(a) Phototransistor

(b) Full adder

(c) N -type semiconductor

(d) Registers